

Test Tuesday 5/15

- Electrostatics
- Circuits

Electric field equation:

$$E = \frac{k|q|}{r^2}$$

this gives the magnitude

direction comes from arrows of
the electric field

- if there are multiple charges,
we must calculate an electric
field from each charge


Resistors:

- The point is to control current
- Two main ways to connect pieces:

1. Series



2. Parallel (branching)

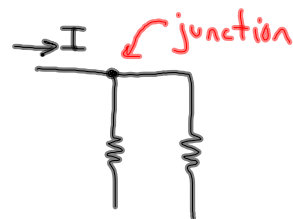

- There is a relationship between voltage, current, and resistance:


$$V = IR \rightarrow \text{resistance}$$

\hookrightarrow voltage \hookrightarrow current

Ohm's Law


- Equivalent resistance:

- Series:

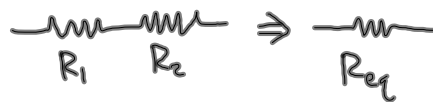


$$R_{eq} = R_1 + R_2$$

- Parallel:

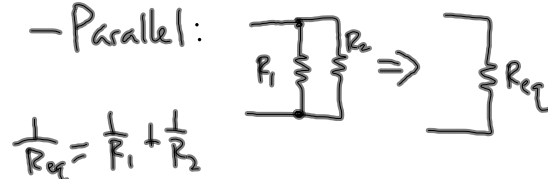

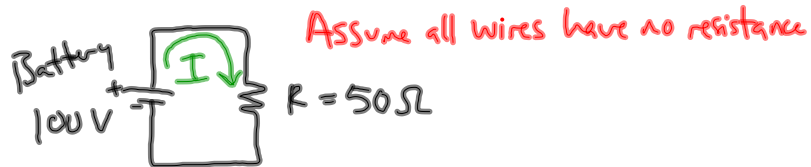
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$V = IR$$
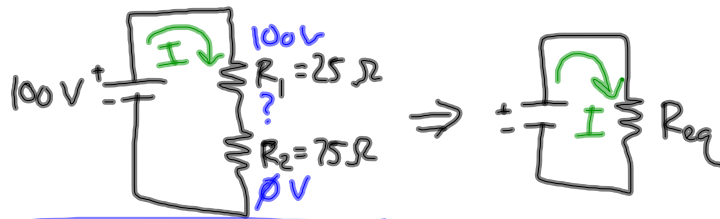
$$I = \frac{V}{R} = \frac{100\text{V}}{50\Omega} = 2\text{A}$$



Pieces in series
share current.
They have different
voltage drops.

$$\begin{aligned} R_{eq} &= R_1 + R_2 \\ &= 25\Omega + 75\Omega \\ &= 100\Omega \end{aligned}$$

$$I_{\text{total}} = \frac{V_{\text{battery}}}{R_{eq}} = \frac{100\text{V}}{100\Omega} = 1\text{A}$$


$$V_1 = I_{\text{total}} R_1 = (1\text{A})(25\Omega) = 25\text{V}$$

$$V_2 = I_{\text{total}} R_2 = (1\text{A})(75\Omega) = 75\text{V}$$

$$V_1 + V_2 = V_{\text{battery}}$$

$$25\text{V} + 75\text{V} = 100\text{V} \quad \checkmark$$

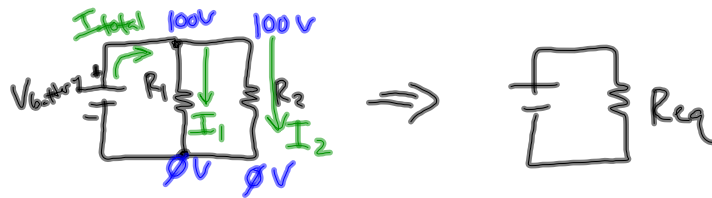All voltage drops must add together
to equal the voltage gain.



$$V_{\text{battery}} = 100 \text{ V}$$

$$R_1 = 25 \Omega$$

$$R_2 = 75 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \left[\frac{1}{25 \Omega} + \frac{1}{75 \Omega} \right]^{-1}$$

$$\text{calculator: } \left(\left(\frac{1}{25} \right) + \left(\frac{1}{75} \right) \right)^{-1}$$

$$R_{eq} = 18.75 \Omega$$

Pieces in parallel share voltage.
They have different currents.

$$I_{\text{total}} = \frac{V_{\text{battery}}}{R_{eq}} = \frac{100 \text{ V}}{18.75 \Omega} = 5.33 \text{ A}$$

$$I_1 = \frac{V_{\text{battery}}}{R_1} = \frac{100 \text{ V}}{25 \Omega} = 4 \text{ A}$$


$$I_2 = \frac{V_{\text{battery}}}{R_2} = \frac{100 \text{ V}}{75 \Omega} = 1.33 \text{ A}$$

$$I_1 + I_2 = I_{\text{total}}$$


$$4 \text{ A} + 1.33 \text{ A} = 5.33 \text{ A} \quad \checkmark$$

Current in each branch must equal
the current coming into the branches.


Equivalent Resistance Practice:

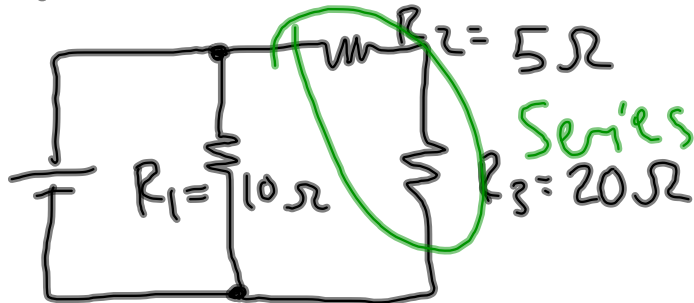

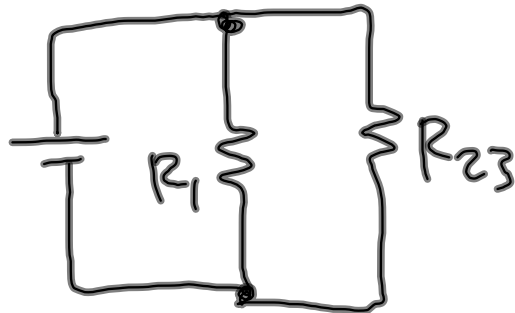Start outside and work in \rightarrow farthest away from battery




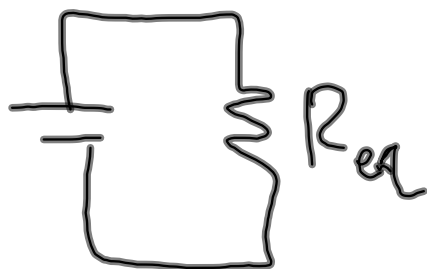
$$\begin{aligned} R_{23} &= R_2 + R_3 \\ &= 5\ \Omega + 20\ \Omega \\ &= 25\ \Omega \end{aligned}$$




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_{23}}$$

$$R_{eq} = 7.14\ \Omega$$

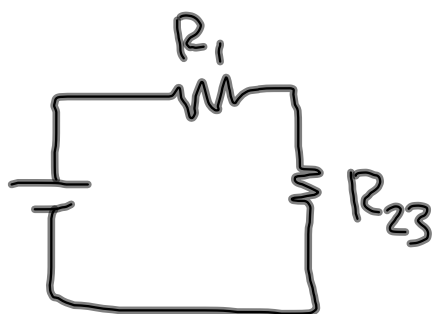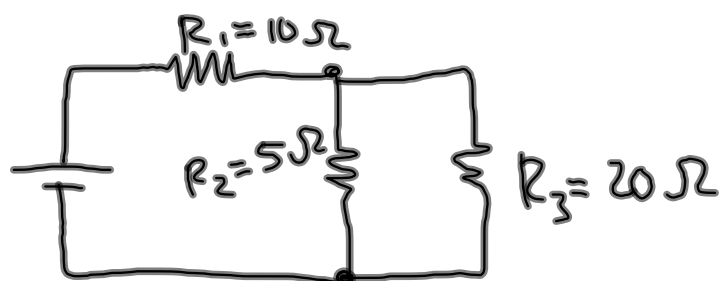

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{23} = 4\ \Omega$$

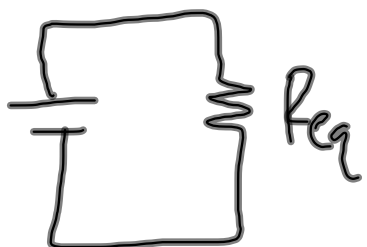

$$\begin{aligned} R_{eq} &= R_1 + R_{23} \\ &= 10\ \Omega + 4\ \Omega \\ &= 14\ \Omega \end{aligned}$$

Electric Power:

$$P = IV$$

unit is still Watts

$$P = I^2 R = \frac{V^2}{R}$$